

**Trainer Module: ETEK ACS-3000-02**

# **Chapter Three**

## **AM Modulator**

**ETEK TECHNOLOGY CO., LTD.**

**E-mail: [etek21@ms59.hinet.net](mailto:etek21@ms59.hinet.net)**

**http: // [www.etek21.com.tw](http://www.etek21.com.tw)**



## 3-1: Curriculum Objectives

1. To understand the basic theory of amplitude modulation (AM).
2. To understand the waveform and frequency spectrum of AM modulator, also calculate the percentage of modulation.
3. To design and implement the AM modulator by using transistor.
4. To design and implement the AM modulator by balanced modulator.
5. To understand the measurement and adjustment of AM modulator.

## 3-2: Curriculum Theory

In amplitude modulation (AM), we utilize the amplitude of audio signal to modulate the amplitude of carrier signal, which means that the amplitude of carrier signal will be varied with amplitude of audio signal. The waveform of AM modulation is shown in figure 3-1 and its block diagram is shown in figure 3-2. In figure 3-2, we know that in order to generate the AM signal, we just need to add a DC signal with the audio signal, and then multiply the added signal with the carrier signal.

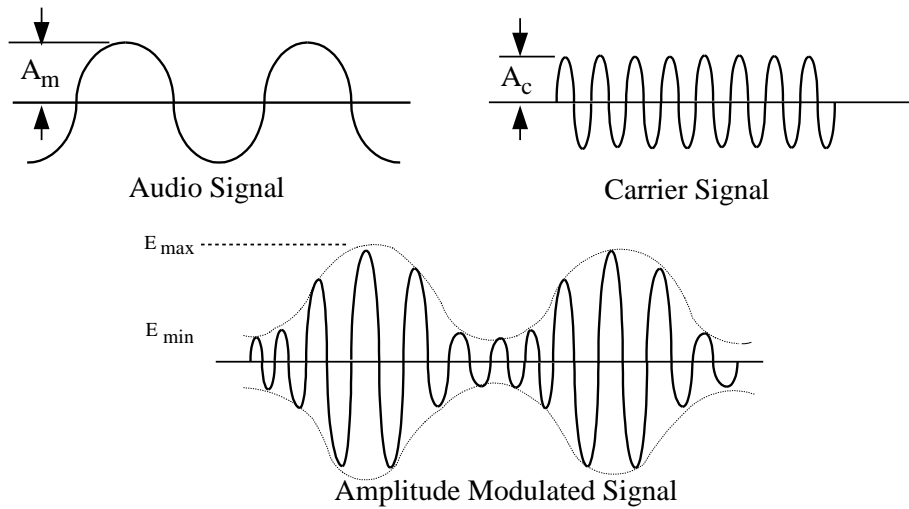


Figure 3-1 Signal waveform of amplitude modulation.

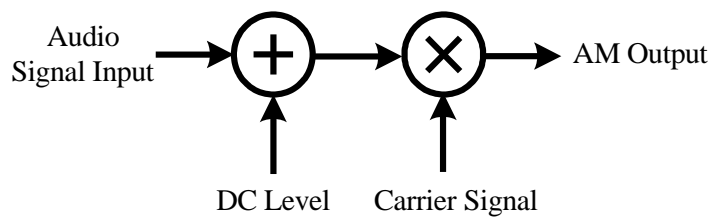


Figure 3-2 Block diagram of AM modulator.

Let the audio signal be  $A_m \cos(2\pi f_m t)$  and carrier signal be  $A_c \cos(2\pi f_c t)$ , then the amplitude modulation can be expressed as

$$\begin{aligned} x_{AM}(t) &= [A_{DC} + A_m \cos(2\pi f_m t)] A_c \cos(2\pi f_c t) \\ &= A_{DC} A_c [1 + m \cos(2\pi f_m t)] \cos(2\pi f_c t) \end{aligned} \quad (3-1)$$

Where



$$m = A_m / A_{DC}.$$

$A_{DC}$  : DC signal magnitude.

$A_m$  : Audio signal amplitude.

$A_C$  : Carrier signal amplitude.

$f_m$  : Audio signal frequency.

$f_C$  : Carrier signal frequency.

$m$ : Modulation index or depth of modulation.

From equation (3-1), we notice that the variation of the magnitude  $A_{DC} A_C [1 + m \cos(2\pi f_m t)]$  of the carrier signal can be controlled by parameter “m”. This means that we can change the magnitude of the audio signal ( $A_m$ ) or DC signal ( $A_{DC}$ ) to control the level or depth of the carrier signal. Therefore, this parameter “m” is known as the modulation index.

Besides, we can also rewrite equation (3-1) as

$$\begin{aligned} x_{AM}(t) = \frac{1}{2} A_{DC} A_C m \{ \cos [2\pi(f_c + f_m) t] + \cos [2\pi(f_c - f_m) t] \} \\ + A_{DC} A_C \cos (2\pi f_c t) \end{aligned} \quad (3-2)$$

The first term represents double sideband signals; the second term represents carrier signal. From equation (3-2), we can sketch the frequency spectrum of amplitude modulation as shown in figure 3-3. Since the audio

signal is hidden in the double sidebands and the carrier signal does not contain any message, therefore the power is consumed in carrier during transmission of amplitude modulation signal. For this reason, the transmission efficiency of AM modulation is lower than double sidebands suppressed carrier (DSB-SC) modulation but its demodulation circuit is much simpler.

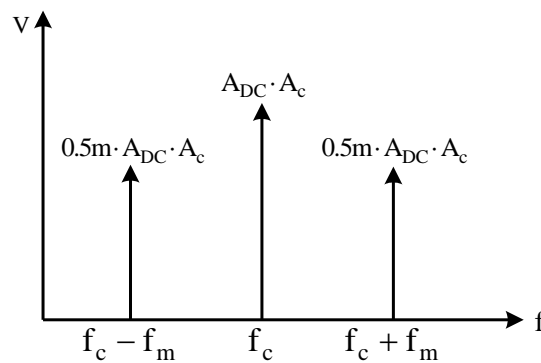


Figure 3-3 Frequency spectrum of amplitude modulation signal.

There is an important parameter “m” in equation (3-1) called modulation index or depth of modulation. Normally it is represented in percentage, so we also call modulation percentage. Modulation index is an important parameter in equation (3-1). The definition is as follow

$$m = \frac{\text{Audio signal amplitude}}{\text{DC signal magnitude}} \times 100 \% = \frac{A_m}{A_{DC}} \times 100 \% \quad (3-3)$$

Generally, the magnitude of DC signal is not easy to measure; therefore, we express the modulation index in another form



$$m = \frac{E_{\max} - E_{\min}}{E_{\max} + E_{\min}} \times 100 \% \quad (3-4)$$

Where  $E_{\max}$  and  $E_{\min}$  as shown in figure 3-1 are  $E_{\max} = A_C + A_m$  and  $E_{\min} = A_C - A_m$ .

We know that at amplitude modulation, the audio signal is hidden in the double sidebands, so if the double sideband signals are getting stronger, the transmission efficiency is getting better. From equation (3-2), we know that the double sideband signals are proportional to the modulation index. Thus, the larger the modulation index, the better the transmission efficiency.

Normally modulation index is smaller or equal to 1. If greater than 1, we call it over modulation, as shown in figure 3-4. Figure 3-4 shows the waveforms of the over modulation. In figure 3-4, we can see that the variation of carrier signal is no longer a sinusoidal wave. It is rather a distorted sinusoidal wave, therefore, this kind of AM signal is unable to demodulate and recover to the original by using the envelop detection in next chapter.

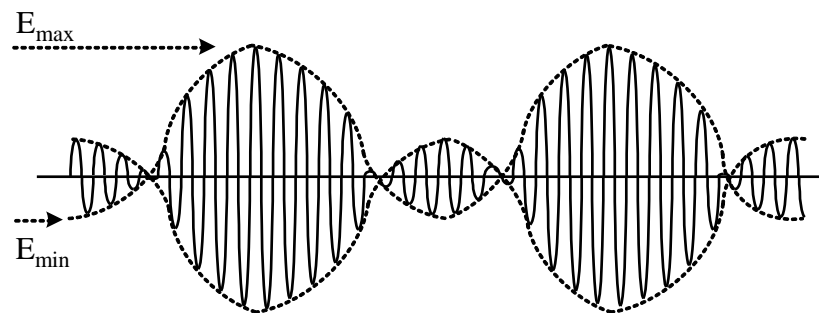


Figure 3-4 Waveforms of the over modulation.



As we know that the AM modulator can be implemented by using a multiplier. However, in electronics circuit, the multiplier is constructed by the nonlinear characteristics of active component. Therefore, in this chapter, we will discuss the design of AM modulator by using a single transistor and balanced modulator.

### 3-1 Transistor AM Modulator

The circuit diagram of transistor AM modulator is shown in figure 3-5. In figure 3-5, the audio signal ( $A_m \cos(2\pi f_m t)$ ) will pass through a transformer and send into the base of the transistor. The carrier signal ( $A_c \cos(2\pi f_c t)$ ) also passes through a transformer and sends into the emitter of the transistor. These two signals will form a small amount of small signal voltage difference at the base and emitter of the transistor. The small signal voltage difference is

$$V_{be} = V_b - V_e = A_m \cos(2\pi f_m t) - A_c \cos(2\pi f_c t) \quad (3-5)$$

Then at the collector of the transistor, this voltage difference will produce a small signal collector current as

$$I_c = I_s e^{V_{be}/V_T} \quad (3-6)$$

Expand equation (3-6) by Taylor's expansion, then we get

$$I_c = aV_{be} + bV_{be}^2 \quad (3-7)$$

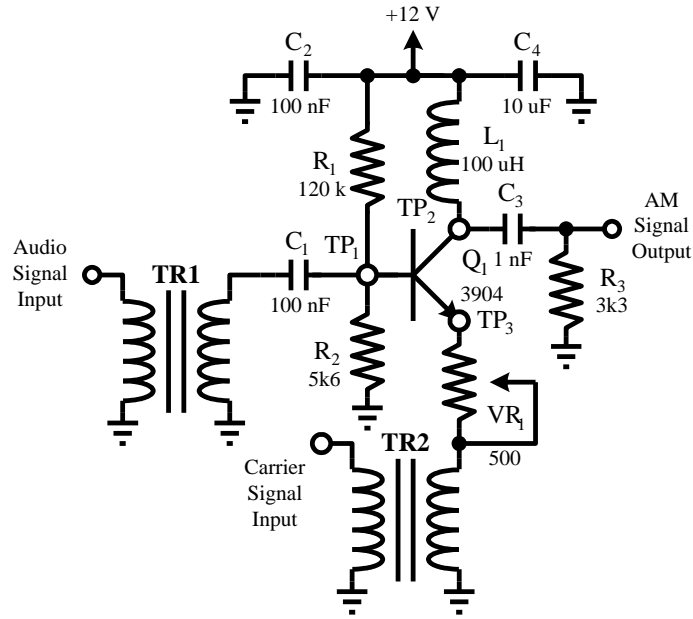


Figure 3-5 Circuit diagram of transistor AM modulator.

In equation (3-7), we notice that after the audio signal and the carrier signal input into the base and collector of the transistor, we can obtain  $\cos^2(2\pi f_m t)$ ,  $\cos^2(2\pi f_c t)$  and  $\cos(2\pi f_m t) \times \cos(2\pi f_c t)$  signals at the collector. Then we utilize the filter to obtain the modulated AM signal  $\cos(2\pi f_m t) \times \cos(2\pi f_c t)$ . In figure 3-5, the inductor  $L_1$ , capacitor  $C_3$  and resistor  $R_3$  comprise a high-pass filter, which is used to obtain the modulated AM signal. Capacitor  $C_1$  is the coupling capacitor. Capacitor  $C_2$  and  $C_3$  are the bypass capacitors. Resistors  $R_1$  and  $R_2$  are the bias resistors. Variable resistor  $VR_1$  is used to change the operation point of the transistor and it also used to control the magnitude of the carrier, which inputs into the collector of the transistor. Therefore, it can adjust the output signal waveform of the modulator.



### 3-2 MC1496 AM Modulator

The main different between the design of AM modulator by using balanced modulator and the transistor is that we can use the theory of balanced modulator to cancel out the unwanted harmonics signals, which is produced by the nonlinear characteristic of the transistor, then the remain signal is the AM signal. In this chapter, we utilize the balanced modulator (MC1496) to implement the AM modulator.

Follow the variation of input signal frequency, the balanced modulator (MC1496) can become a frequency multiplier, AM modulator or double sidebands suppressed carrier modulator (DSB-SC Modulator). Its input signal, output signal and circuit characteristics are shown in table 3-1.

Table 3-1 Three different types of modulation signal produced by different signals frequency of balanced modulator.

Input Carrier Signal	Input Audio Signal	Output Balanced Modulator	Circuit Characteristics
$f_c$	$f_c$	$2f_c$	Frequency Multiplier
$f_c$	$f_m$	$f_c, f_c + f_m, f_c - f_m$	Amplitude Modulator
$f_c$	$f_m$	$f_c + f_m, f_c - f_m$	DSB-SC Modulator



Figure 3-6 is the internal circuit diagram of MC1496, where  $D_1$ ,  $R_1$ ,  $R_2$ ,  $R_3$ ,  $Q_7$  and  $Q_8$  comprise an electric current source, which can supply DC bias current for  $Q_5$  and  $Q_6$ .  $Q_5$  and  $Q_6$  comprise a differential combination to drive the dual differential amplifiers constructed by  $Q_1$ ,  $Q_2$ ,  $Q_3$  and  $Q_4$ . Pin 1 and 4 are the inputs of audio signal, after that this signal will be amplified by the differential amplifier, which is comprised by  $Q_5$  and  $Q_6$ . Pin 8 and 10 are the inputs of carrier signal. Then the amplified audio signal will multiply by the carrier signal at the dual differential amplifiers constructed by  $Q_1$ ,  $Q_2$ ,  $Q_3$  and  $Q_4$ . Finally, the output signals can be obtained at the collectors of  $Q_1$ ,  $Q_2$ ,  $Q_3$  and  $Q_4$ , respectively. The resistor between pins 2 and 3 controls the gain of the balanced modulator; the resistor of pin 5 determines the magnitude of bias current for amplifier.

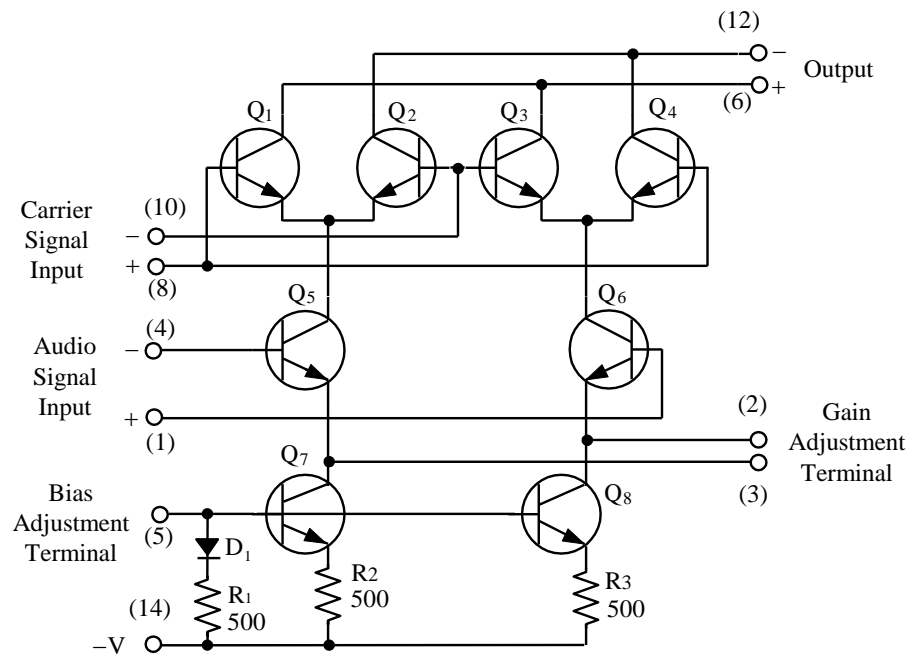


Figure 3-6 Internal circuit diagram of MC1496.

Figure 3-7 is the circuit diagram of AM modulator by utilizing MC1496. We can see that the carrier signal and audio signal belong to single ended input. The carrier signal input from pin 10 and the audio signal input from pin 1. Therefore,  $R_8$  determine the gain of the whole circuit and  $R_9$  determine the magnitude of bias current. If we adjust the variable resistor  $VR_1$  or change the input amplitude of audio signal, then we can control the percentage modulation of AM modulator.

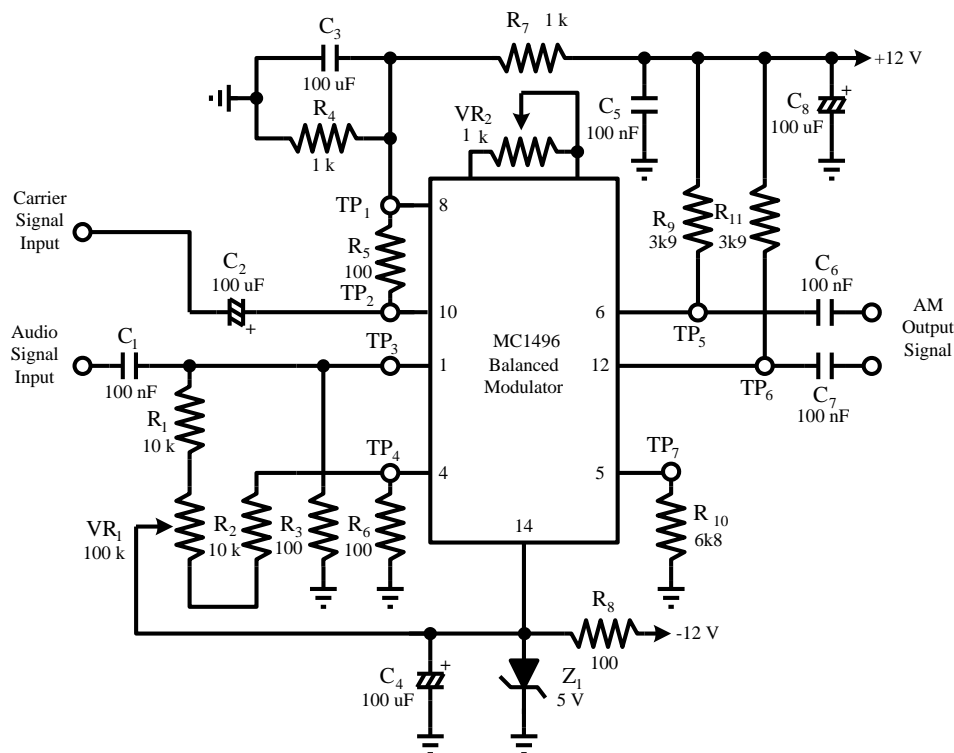


Figure 3-7 Circuit diagram of amplitude modulator by utilizing MC1496.



## 3-3: Experiment Items

### Experiment 1: Transistor AM modulator

1. Refer to the circuit diagram in figure 3-5 or figure ACS3-1 on ETEK ACS-3000-02 module.
2. At audio signal input port (Audio I/P), input 150 mV<sub>pp</sub> amplitude, 1 kHz sine wave frequency; at carrier signal input port (Carrier I/P), input 300 mV<sub>pp</sub> amplitude, 500 kHz sine wave frequency.
3. By using oscilloscope, observe on output signal waveforms of AM output port (AM O/P). Adjust VR<sub>1</sub> so that the modulated AM signal is maximum without distortion. Then records the measured results in table 3-2.
4. By using oscilloscope, observe on output signal waveforms of the base (TP1) and collector (TP2) of the transistor. Then record the measured results in table 3-2.
5. By using oscilloscope, observe on output signal waveforms of the mixing (TP3) of the transistor. Then record the measured results in table 3-2.
6. By using spectrum analyzer, observe on the frequency spectrum of AM O/P and TP2. Then record the measured results in table 3-2.
7. Substitute the measured results into equation (3-4), find the modulation percentage and record in table 3-2.

8. According to the input signals in table 3-2, repeat step 4 to 7 and record the measured results in table 3-2.
9. According to the input signals in table 3-3, repeat step 2 to 7 and record the measured results in table 3-3.

## **Experiment 2: MC1496 AM modulator**

### **Experiment 2-1: Observe on the variation of AM modulator by changing the amplitude and frequency of audio signal**

1. Refer to the circuit diagram in figure 3-7 or figure ACS3-2 on ETEK ACS-3000-02 module. Let J1 be short circuit, J2 be open circuit; i.e.  $R_{10} = 6.8 \text{ k}\Omega$ .
2. At audio signal input port (Audio I/P), input  $600 \text{ mV}_{\text{pp}}$  amplitude, 1 kHz sine wave frequency; at carrier signal input port (Carrier I/P), input  $300 \text{ mV}_{\text{pp}}$  amplitude, 500 kHz sine wave frequency.
3. By using oscilloscope, observe on output signal waveforms of AM output ports (AM O/P1 and AM O/P2). Adjust  $\text{VR}_2$  so that the signal at AM O/P1 is maximum without distortion. Adjust  $\text{VR}_1$  so that the modulation index of the AM signal reach 50 %. Then records the measured results in table 3-4.
4. By using oscilloscope, observe on input signal waveforms of the pin 8 (TP1), pin 10 (TP2), pin 1 (TP3), and pin 4 (TP4) of the balanced modulator. Then record the measured results in table 3-4.



5. By using oscilloscope, observe on output signal waveforms of the mixing (TP5 and TP6) of the balanced modulator and the bias operation point (TP7). Then record the measured results in table 3-4.
6. By using spectrum analyzer, observe on the frequency spectrum of AM O/P1, AM O/P2, TP5 and TP6. Then record the measured results in table 3-4.
7. Substitute the measured results into equation (3-4), find the modulation percentage and record in table 3-4.
8. According to the input signals in table 3-4, repeat step 4 to 7 and record the measured results in table 3-4.
9. Let J1 be open circuit and J2 be short circuit, i.e. change the resistor  $R_{10} = 6.8 \text{ k}\Omega$  to  $R_{12} = 3.3 \text{ k}\Omega$ . Repeat step 2 to step 8 and record the measured results in table 3-5.
10. According to the input signals in table 3-6, repeat step 2 to 7 and record the measured results in table 3-6.

**Experiment 2-2: Observe on the variation of AM modulator  
by changing the amplitude and frequency  
of carrier signal**

1. Refer to the circuit diagram in figure 3-7 or figure ACS3-2 on ETEK ACS-3000-02 module. Let J1 be open circuit, J2 be short circuit; i.e.  $R_{12} = 3.3 \text{ k}\Omega$ .

2. At audio signal input port (Audio I/P), input 600 mV<sub>pp</sub> amplitude, 1 kHz sine wave frequency; at carrier signal input port (Carrier I/P), input 200 mV<sub>pp</sub> amplitude, 500 kHz sine wave frequency.
3. By using oscilloscope, observe on output signal waveforms of AM output ports (AM O/P1 and AM O/P2). Adjust VR<sub>2</sub> so that the signal at AM O/P1 is maximum without distortion. Adjust VR<sub>1</sub> so that the modulation index of the AM signal reach 50 %. Then records the measured results in table 3-7.
4. By using oscilloscope, observe on output signal waveforms of the pin 8 (TP1), pin 10 (TP2), pin 1 (TP3), and pin 4 (TP4) of the balanced modulator. Then record the measured results in table 3-7.
5. By using oscilloscope, observe on output signal waveforms of the mixing (TP5 and TP6) of the balanced modulator and the bias operation point (TP7). Then record the measured results in table 3-7.
6. By using spectrum analyzer, observe on the frequency spectrum of AM O/P1, AM O/P2, TP5 and TP6. Then record the measured results in table 3-7.
7. Substitute the measured results into equation (3-4), find the modulation percentage and record in table 3-7.
8. According to the input signals in table 3-7, repeat step 4 to 7 and record the measured results in table 3-7.
9. According to the input signals in table 3-8, repeat step 2 to 7 and record the measured results in table 3-8.



### **Experiment 2-3: Observe on the variation of AM modulator by changing the variable resistor $VR_1$**

1. Refer to the circuit diagram in figure 3-7 or figure ACS3-2 on ETEK ACS-3000-02 module. Let J1 be open circuit, J2 be short circuit; i.e.  $R_{12} = 3.3 \text{ k}\Omega$ .
2. At audio signal input port (Audio I/P), input  $600 \text{ mV}_{pp}$  amplitude,  $1 \text{ kHz}$  sine wave frequency; at carrier signal input port (Carrier I/P), input  $300 \text{ mV}_{pp}$  amplitude,  $500 \text{ kHz}$  sine wave frequency.
3. By using oscilloscope, observe on output signal waveforms of AM output ports (AM O/P1 and AM O/P2). Adjust  $VR_1$  so that the modulation index of the AM signal reach 30 %. Then records the measured results in table 3-9.
4. By using spectrum analyzer, observe on the frequency spectrum of AM O/P1 and AM O/P2. Then record the measured results in table 3-9.
5. Substitute the measured results into equation (3-4), find the modulation percentage and record in table 3-9.
6. According to the input signals in table 3-9, repeat step 2 to 5 and record the measured results in table 3-9.



### **Experiment 2-4: Observe on the variation of AM modulator by changing the variable resistor VR<sub>2</sub>**

1. Refer to the circuit diagram in figure 3-7 or figure ACS3-2 on ETEK ACS-3000-02 module. Let J1 be open circuit, J2 be short circuit; i.e.  $R_{12} = 3.3 \text{ k}\Omega$ .
2. At audio signal input port (Audio I/P), input  $600 \text{ mV}_{pp}$  amplitude, 1 kHz sine wave frequency; at carrier signal input port (Carrier I/P), input  $300 \text{ mV}_{pp}$  amplitude, 500 kHz sine wave frequency.
3. By using oscilloscope, observe on output signal waveforms of AM output ports (AM O/P1 and AM O/P2). Adjust VR<sub>1</sub> so that the modulation index of the AM signal reach 50 %.
4. Adjust VR<sub>2</sub> so that the resistance is  $100 \Omega$ ,  $300 \Omega$  and  $800 \Omega$ , the others remain. Then record the measured results in table 3-10.



## 3-4: Experimental Results

### Experiment 1: Transistor AM modulator

Table 3-2 Observe on the variation of amplitude modulation by changing the amplitude of audio signal ( $f_m = 1$  kHz,  $f_c = 500$  kHz,  $V_c = 300$  mV).

Output Signal Ports	Audio Signal Amplitudes	
	100 mV <sub>pp</sub>	150 mV <sub>pp</sub>
AM O/P		
TP1		
TP2		
TP3		
AM O/P Output Signal Spectrums		
TP2 Output Signal Spectrums		
Modulation Index	$E_{\max} = \underline{\hspace{1cm}}$ $E_{\min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}}\%$	$E_{\max} = \underline{\hspace{1cm}}$ $E_{\min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}}\%$

Table 3-3 Observe on the variation of amplitude modulation by changing the frequency of audio signal ( $V_m = 200 \text{ mV}_{pp}$ ,  $f_c = 500 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ).

Output Signal Ports	Audio Signal Frequencies	
	100 Hz	400 Hz
AM O/P		
TP1		
TP2		
TP3		
AM O/P Output Signal Spectrums		
TP2 Output Signal Spectrums		
Modulation Index	$E_{\max} = \underline{\hspace{1cm}}$ $E_{\min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}}\%$	$E_{\max} = \underline{\hspace{1cm}}$ $E_{\min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}}\%$

**Experiment 2: MC1496 AM modulator**

Table 3-4 Observe on the variation of amplitude modulation by changing the amplitude of audio signal ( $f_m = 1 \text{ kHz}$ ,  $f_c = 500 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $R_{10} = 6.8 \text{ k}\Omega$ ).

Output Signal Ports	Audio Signal Amplitudes	
	600 mV <sub>pp</sub>	300 mV <sub>pp</sub>
AM O/P1		
AM O/P2		
TP1		
TP2		

Table 3-4 Observe on the variation of amplitude modulation by changing the amplitude of audio signal (Continue) ( $f_m = 1 \text{ kHz}$ ,  $f_c = 500 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $R_{10} = 6.8 \text{ k}\Omega$ ).

Output Signal Ports	Audio Signal Amplitudes	
	$600 \text{ mV}_{pp}$	$300 \text{ mV}_{pp}$
TP3		
TP4		
TP5		
TP6		



Table 3-4 Observe on the variation of amplitude modulation by changing the amplitude of audio signal (Continue) ( $f_m = 1 \text{ kHz}$ ,  $f_c = 500 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $R_{10} = 6.8 \text{ k}\Omega$ ).

Output Signal Ports	Audio Signal Amplitudes	
	600 mV <sub>pp</sub>	300 mV <sub>pp</sub>
TP7		
AM O/P1 Output Signal Spectrums		
AM O/P2 Output Signal Spectrums		
TP5 Output Signal Spectrums		
TP6 Output Signal Spectrums		
Modulation Index	$E_{\max} = \underline{\hspace{1cm}}$ $E_{\min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}}\%$	$E_{\max} = \underline{\hspace{1cm}}$ $E_{\min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}}\%$

Table 3-5 Observe on the variation of amplitude modulation by changing the amplitude of audio signal ( $f_m = 1 \text{ kHz}$ ,  $f_c = 500 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).

Output Signal Ports	Audio Signal Amplitudes	
	$600 \text{ mV}_{pp}$	$300 \text{ mV}_{pp}$
AM O/P1		
AM O/P2		
TP1		
TP2		

Notice : The amplitude of measured signals on the test points of TP1, TP4 and TP5 would be very small, you may need a precision oscilloscope to measure those test points. Or you can ignore these steps of experiment item, and go to the next step.



Table 3-5 Observe on the variation of amplitude modulation by changing the amplitude of audio signal (Continue) ( $f_m = 1 \text{ kHz}$ ,  $f_c = 500 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).

Output Signal Ports	Audio Signal Amplitudes	
	600 mV <sub>pp</sub>	300 mV <sub>pp</sub>
TP3		
TP4		
TP5		
TP6		



Table 3-5 Observe on the variation of amplitude modulation by changing the amplitude of audio signal (Continue) ( $f_m = 1 \text{ kHz}$ ,  $f_c = 500 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).

Output Signal Ports	Audio Signal Amplitudes	
	600 mV <sub>pp</sub>	300 mV <sub>pp</sub>
TP7		
AM O/P1 Output Signal Spectrums		
AM O/P2 Output Signal Spectrums		
TP5 Output Signal Spectrums		
TP6 Output Signal Spectrums		
Modulation Index	$E_{\max} = \underline{\hspace{1cm}}$ $E_{\min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}}\%$	$E_{\max} = \underline{\hspace{1cm}}$ $E_{\min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}}\%$



Table 3-6 Observe on the variation of amplitude modulation by changing the frequency of audio signal ( $V_m = 600 \text{ mV}_{pp}$ ,  $f_c = 500 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).

Output Signal Ports	Audio Signal Frequencies	
	1 kHz	2 kHz
AM O/P1		
AM O/P2		
TP1		
TP2		

Notice : The amplitude of measured signals on the test points of TP1, TP4 and TP5 would be very small, you may need a precision oscilloscope to measure those test points. Or you can ignore these steps of experiment item, and go to the next step.

Table 3-6 Observe on the variation of amplitude modulation by changing the frequency of audio signal (Continue) ( $V_m = 600 \text{ mV}_{pp}$ ,  $f_c = 500 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).

Output Signal Ports	Audio Signal Frequencies	
	1 kHz	2 kHz
TP3		
TP4		
TP5		
TP6		



Table 3-6 Observe on the variation of amplitude modulation by changing the frequency of audio signal (Continue) ( $V_m = 600 \text{ mV}_{pp}$ ,  $f_c = 500 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).

Output Signal Ports	Audio Signal Amplitudes	
	$600 \text{ mV}_{pp}$	$300 \text{ mV}_{pp}$
TP7		
AM O/P1 Output Signal Spectrums		
AM O/P2 Output Signal Spectrums		
TP5 Output Signal Spectrums		
TP6 Output Signal Spectrums		
Modulation Index	$E_{max} = \underline{\hspace{1cm}}$ $E_{min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}}\%$	$E_{max} = \underline{\hspace{1cm}}$ $E_{min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}}\%$

Table 3-7 Observe on the variation of amplitude modulation by changing the amplitude of carrier signal ( $V_m = 600 \text{ mV}_{pp}$ ,  $f_m = 1 \text{ kHz}$ ,  $f_c = 500 \text{ kHz}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).

Output Signal Ports	Carrier Signal Amplitudes	
	200 mV <sub>pp</sub>	300 mV <sub>pp</sub>
AM O/P1		
AM O/P2		
TP3		
TP4		

Notice : The amplitude of measured signals on the test points of TP1, TP4 and TP5 would be very small, you may need a precision oscilloscope to measure those test points. Or you can ignore these steps of experiment item, and go to the next step.



Table 3-7 Observe on the variation of amplitude modulation by changing the amplitude of carrier signal (Continue) ( $V_m = 600 \text{ mV}_{pp}$ ,  $f_m = 1 \text{ kHz}$ ,  $f_c = 500 \text{ kHz}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).

Output Signal Ports	Carrier Signal Amplitudes	
	200 mV <sub>pp</sub>	300 mV <sub>pp</sub>
TP1		
TP2		
TP5		
TP6		

Table 3-7 Observe on the variation of amplitude modulation by changing the amplitude of carrier signal (Continue) ( $V_m = 600 \text{ mV}_{pp}$ ,  $f_m = 1 \text{ kHz}$ ,  $f_c = 500 \text{ kHz}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).

Output Signal Ports	Carrier Signal Amplitudes	
	200 mV <sub>pp</sub>	300 mV <sub>pp</sub>
TP7		
AM O/P1 Output Signal Spectrums		
AM O/P2 Output Signal Spectrums		
TP5 Output Signal Spectrums		
TP6 Output Signal Spectrums		
Modulation Index	$E_{\max} = \underline{\hspace{1cm}}$ $E_{\min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}}\%$	$E_{\max} = \underline{\hspace{1cm}}$ $E_{\min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}}\%$



Table 3-8 Observe on the variation of amplitude modulation by changing the frequency of carrier signal ( $V_m = 600 \text{ mV}_{pp}$ ,  $f_m = 1 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).

Output Signal Ports	Carrier Signal Frequencies	
	500 kHz	1 MHz
AM O/P1		
AM O/P2		
TP3		
TP4		



Table 3-8 Observe on the variation of amplitude modulation by changing the frequency of carrier signal (Continue) ( $V_m = 600 \text{ mV}_{pp}$ ,  $f_m = 1 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).

Output Signal Ports	Carrier Signal Frequencies	
	500 kHz	1 MHz
TP1		
TP2		
TP5		
TP6		



Table 3-8 Observe on the variation of amplitude modulation by changing the frequency of carrier signal (Continue) ( $V_m = 600 \text{ mV}_{pp}$ ,  $f_m = 1 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).

Output Signal Ports	Carrier Signal Frequencies	
	500 kHz	1 MHz
TP7		
AM O/P1 Output Signal Spectrums		
AM O/P2 Output Signal Spectrums		
TP5 Output Signal Spectrums		
TP6 Output Signal Spectrums		
Modulation Index	$E_{\max} = \underline{\hspace{1cm}}$ $E_{\min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}}\%$	$E_{\max} = \underline{\hspace{1cm}}$ $E_{\min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}}\%$

Table 3-9 Observe on the variation of amplitude modulation by changing the variable resistor  $VR_1$  ( $V_m = 600 \text{ mV}_{pp}$ ,  $f_m = 1 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $f_c = 500 \text{ kHz}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).

Modulation Index		Output Signal Waveforms	Output Signal Spectrums	Modulation Percentages
30 %	AM O/P1			$E_{\max} = \underline{\hspace{1cm}}$ $E_{\min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}} \%$
	AM O/P2			$E_{\max} = \underline{\hspace{1cm}}$ $E_{\min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}} \%$
50 %	AM O/P1			$E_{\max} = \underline{\hspace{1cm}}$ $E_{\min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}} \%$
	AM O/P2			$E_{\max} = \underline{\hspace{1cm}}$ $E_{\min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}} \%$
110 %	AM O/P1			$E_{\max} = \underline{\hspace{1cm}}$ $E_{\min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}} \%$
	AM O/P2			$E_{\max} = \underline{\hspace{1cm}}$ $E_{\min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}} \%$



Table 3-10 Observe on the variation of amplitude modulation by changing the variable resistor  $VR_2$  ( $V_m = 600 \text{ mV}_{pp}$ ,  $f_m = 1 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $f_c = 500 \text{ kHz}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).

Magnitudes of Variable Resistor $VR_2$		Output Signal Waveforms	Output Signal Spectrums	Modulation Percentages
100 $\Omega$	AM O/P1			$E_{max} = \underline{\hspace{1cm}}$ $E_{min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}}\%$
	AM O/P2			$E_{max} = \underline{\hspace{1cm}}$ $E_{min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}}\%$
300 $\Omega$	AM O/P1			$E_{max} = \underline{\hspace{1cm}}$ $E_{min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}}\%$
	AM O/P2			$E_{max} = \underline{\hspace{1cm}}$ $E_{min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}}\%$
800 $\Omega$	AM O/P1			$E_{max} = \underline{\hspace{1cm}}$ $E_{min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}}\%$
	AM O/P2			$E_{max} = \underline{\hspace{1cm}}$ $E_{min} = \underline{\hspace{1cm}}$ $m = \underline{\hspace{1cm}}\%$

## 3-5: Problems Discussion

1. Explain the objectives of the transistor  $Q_1$  in figure 3-5.
2. Explain the objectives of the inductor  $L_1$ , capacitor  $C_3$  and resistor  $R_3$  in figure 3-5.
3. Explain the objectives of the variable resistor  $VR_1$  in figure 3-7.
4. Refer to figure 3-7, if we let J2 be short circuit, J1 be open circuit, i.e.  $R_{10}$  changes to  $R_{12}$ , which its value is  $6.8\text{ k}\Omega$  changed to  $3.3\text{ k}\Omega$ . Then describe the variation of the DC bias current of MC1496.
5. Refer to figure 3-7, if we adjust the magnitude of the variable resistor  $VR_2$  from small to large, then describe the variation of the output signal of AM modulator.
6. When modulation index,  $m = 50\%$  and  $110\%$ , what are the ratio of  $E_{\max}$  and  $E_{\min}$ ?











## **Appendix**

# **Expected Experimental Results**

## Chapter 3: Expected Experimental Results

### Experiment 1: Transistor AM modulator

Table 3-2 Observe on the variation of amplitude modulation by changing the amplitude of audio signal ( $f_m = 1 \text{ kHz}$ ,  $f_c = 500 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ).

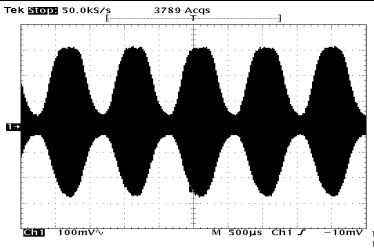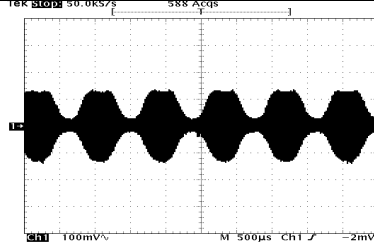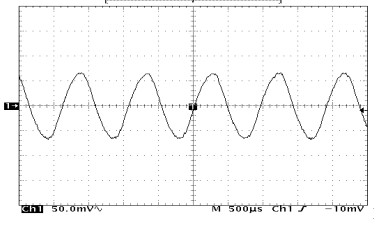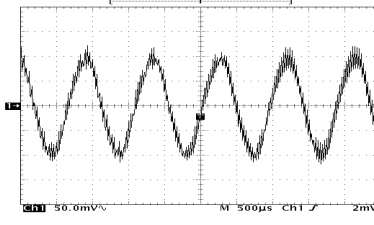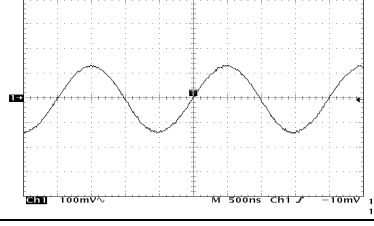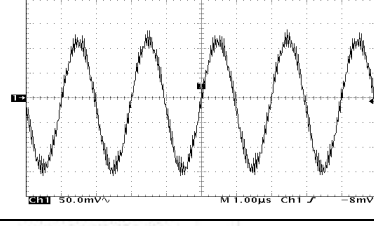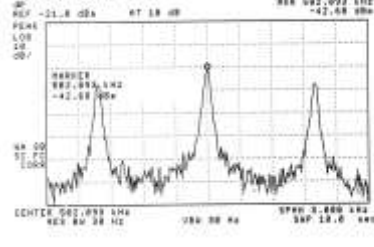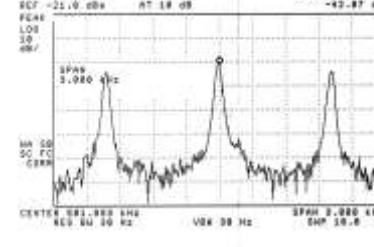Output Signal Ports	Audio Signal Amplitudes	
	100 mV <sub>pp</sub>	150 mV <sub>pp</sub>
AM O/P	 <p>C1 Freq 1.05400KHz C1 Pk-Pk 592mV</p>	 <p>C1 Freq 1.07180KHz Unstable Histogram C1 Pk-Pk 276mV</p>
TP1	 <p>C1 Freq 1.05448KHz C1 Pk-Pk 134mV</p>	 <p>C1 Freq 1.07180KHz Unstable Histogram C1 Pk-Pk 240mV</p>
TP3	 <p>C1 Freq 500.648KHz C1 Pk-Pk 276mV</p>	 <p>C1 Freq 504.948KHz Unstable Histogram C1 Pk-Pk 296mV</p>
AM O/P Output Signal Spectrums	 <p>SPAN 3.000 KHz SMP 10.0 Hz</p>	 <p>SPAN 3.000 KHz SMP 10.0 Hz</p>
Modulation Index	$E_{\max} = 296 \text{ mV}$ $E_{\min} = 50 \text{ mV}$ $m = 71 \%$	$E_{\max} = 138 \text{ mV}$ $E_{\min} = 25 \text{ mV}$ $m = 69 \%$



## Experiment 2: MC1496 AM modulator

Table 3-5 Observe on the variation of amplitude modulation by changing the amplitude of audio signal ( $f_m = 1 \text{ kHz}$ ,  $f_c = 500 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $R_{10} = 3.3 \text{ k}\Omega$ ).









Output Signal Ports	Audio Signal Amplitudes	
	600 mV <sub>pp</sub>	300 mV <sub>pp</sub>
AM O/P1	 <p>C1 Freq = 500.26 kHz Wfm does not cross ref C1 Pk-Pk 1.064 V M 500µs CH1 412mV 29 Nov 2003 11:38:02</p>	 <p>C1 Freq = 500.26 kHz Wfm does not cross ref C1 Pk-Pk 1.42 V M 500µs CH1 490mV 25 Nov 2003 17:28:01</p>
AM O/P2	 <p>C1 Freq = 500.26 kHz Wfm does not cross ref C1 Pk-Pk 1.064 V M 500µs CH1 412mV 29 Nov 2003 11:38:02</p>	 <p>C1 Freq = 500.26 kHz Wfm does not cross ref C1 Pk-Pk 1.48 V M 500µs CH1 490mV 25 Nov 2003 17:28:52</p>
TP1	 <p>C1 Freq = 55.6366 kHz Unstable histogram C1 Pk-Pk 18.6mV M 200µs CH1 60.0mV 29 Nov 2003 11:41:12</p>	 <p>C1 Freq = 499.30 kHz Unstable histogram C1 Pk-Pk 16.00mV M 2.00µs CH1 360µV 25 Nov 2003 17:31:32</p>
TP2	 <p>C1 Freq = 500.26 kHz C1 Pk-Pk 246mV M 1.00µs CH1 3mV 29 Nov 2003 11:42:03</p>	 <p>C1 Freq = 506.07 kHz C1 Pk-Pk 252mV M 2.00µs CH1 0 V 25 Nov 2003 17:32:12</p>



Table 3-5 Observe on the variation of amplitude modulation by changing the amplitude of audio signal (Continue) ( $f_m = 1 \text{ kHz}$ ,  $f_c = 500 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).









Output Signal Ports	Audio Signal Amplitudes	
	600 mV <sub>pp</sub>	300 mV <sub>pp</sub>
TP3	 <p>C1 Freq 1.07528kHz C1 Pk-Pk 210mV</p>	 <p>C1 Freq 1.02828kHz Low signal amplitude C1 Pk-Pk 96mV</p>
TP4	 <p>C1 Freq 4.5290kHz Low signal amplitude C1 Pk-Pk 11.4mV</p>	 <p>C1 Freq 976.97kHz Unstable histogram C1 Pk-Pk 7.68mV</p>
TP5	 <p>C1 Freq <math>\approx \text{Hz}</math> Wfm does not cross ref C1 Pk-Pk 1.112 V</p>	 <p>C1 Freq <math>\approx \text{Hz}</math> Wfm does not cross ref C1 Pk-Pk 1.42 V</p>
TP6	 <p>C1 Freq <math>\approx \text{Hz}</math> Wfm does not cross ref C1 Pk-Pk 1.112 V</p>	 <p>C1 Freq <math>\approx \text{Hz}</math> Wfm does not cross ref C1 Pk-Pk 1.48 V</p>

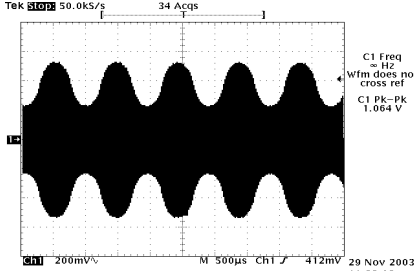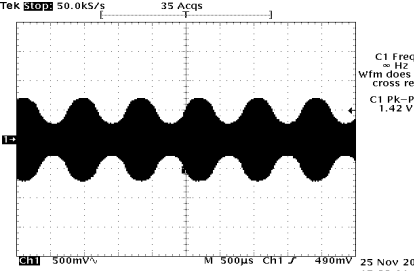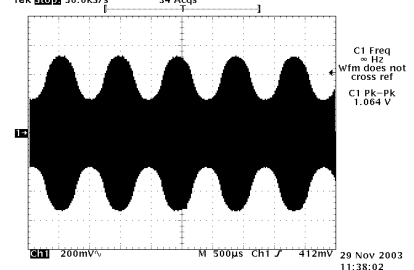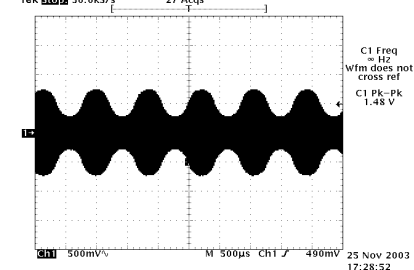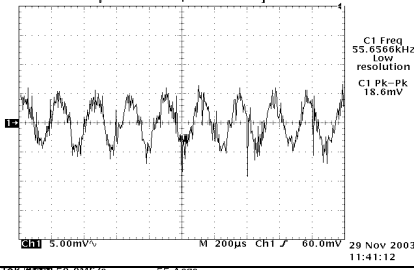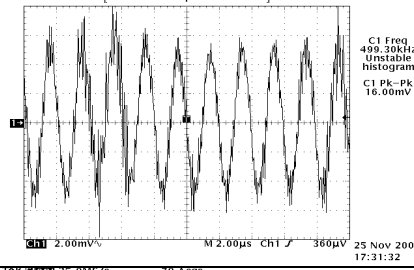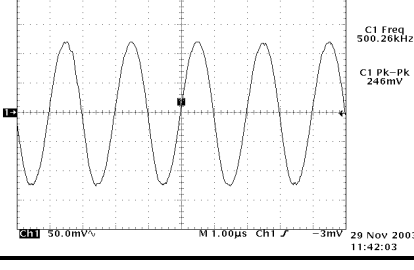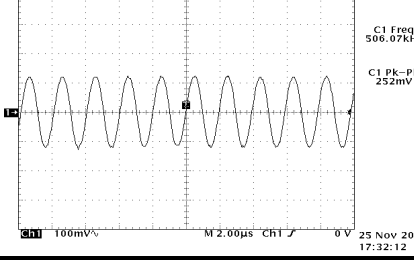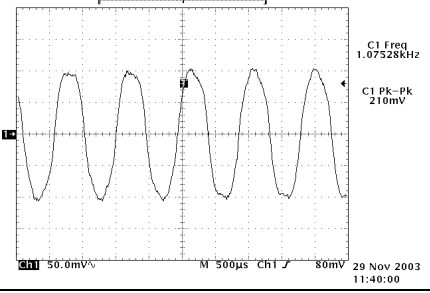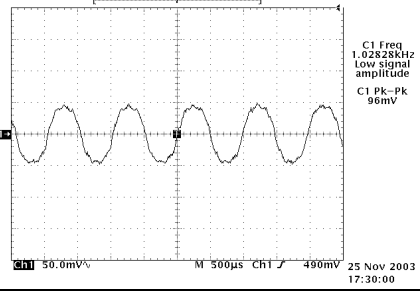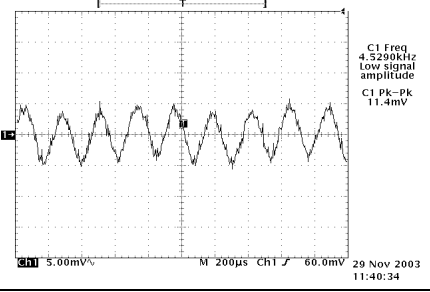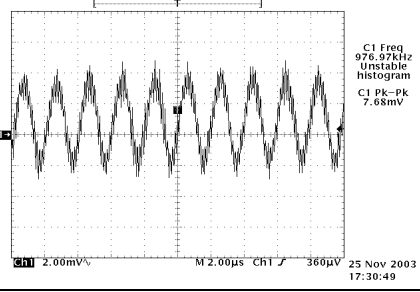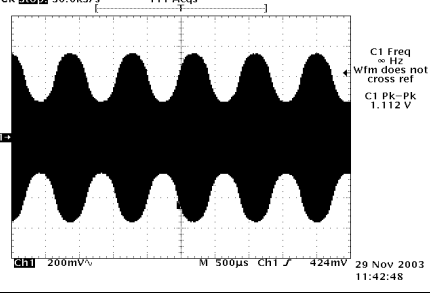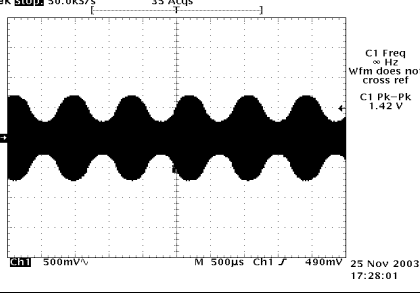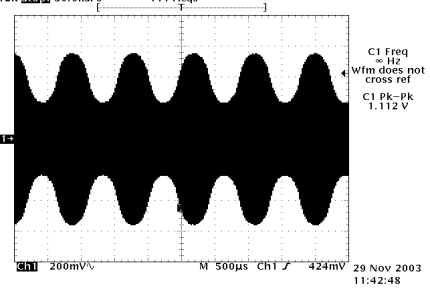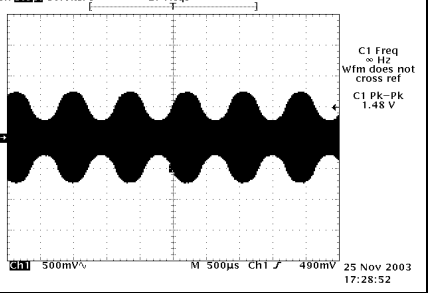

Table 3-5 Observe on the variation of amplitude modulation by changing the amplitude of audio signal (Continue) ( $f_m = 1 \text{ kHz}$ ,  $f_c = 500 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).

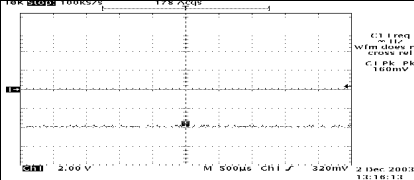
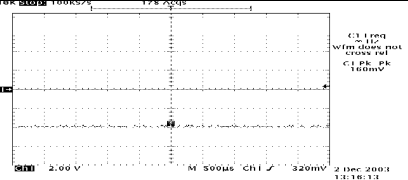
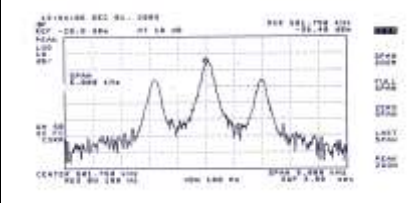
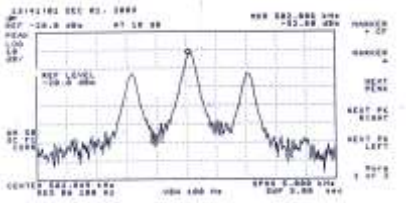
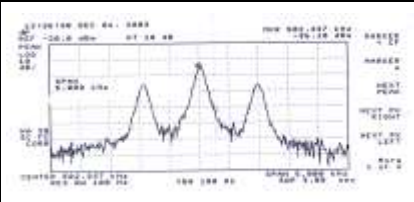

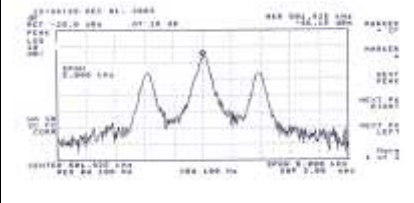
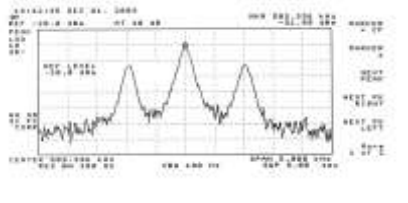
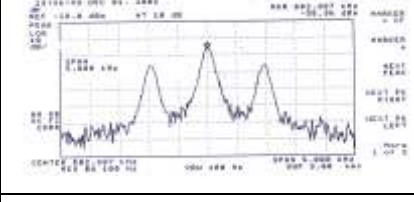
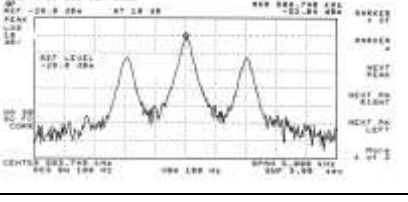
Output Signal Ports	Audio Signal Amplitudes	
	600 mV <sub>pp</sub>	300 mV <sub>pp</sub>
TP7		
AM O/P1 Output Signal Spectrums		
AM O/P2 Output Signal Spectrums		
TP5 Output Signal Spectrums		
TP6 Output Signal Spectrums		
Modulation Index	$E_{\max} = 500 \text{ mV}$ $E_{\min} = 180 \text{ mV}$ $m = 47 \%$	$E_{\max} = 700 \text{ mV}$ $E_{\min} = 250 \text{ mV}$ $m = 47.4 \%$

Table 3-6 Observe on the variation of amplitude modulation by changing the frequency of audio signal ( $V_m = 600 \text{ mV}_{pp}$ ,  $f_c = 500 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).

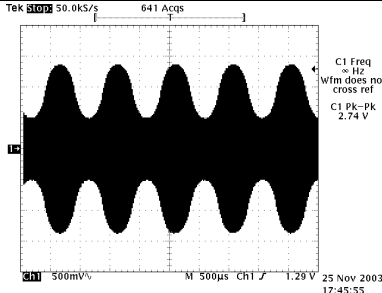
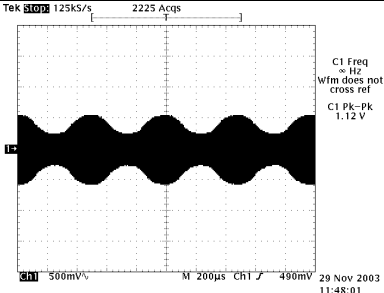
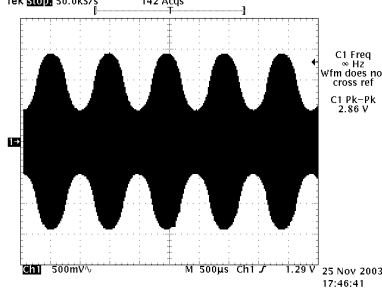
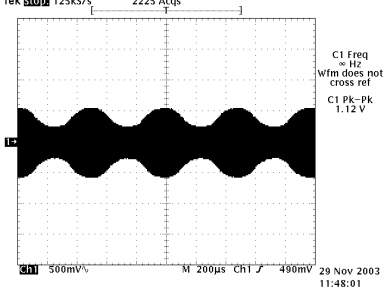
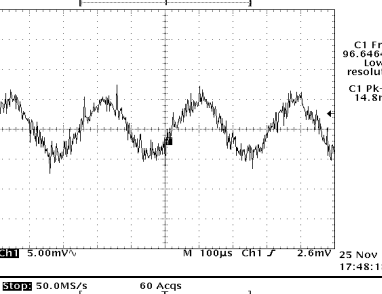
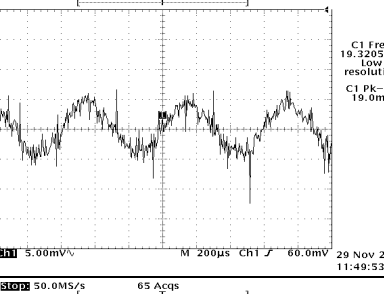
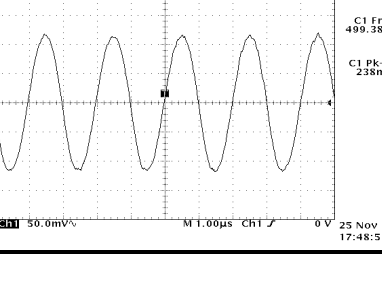
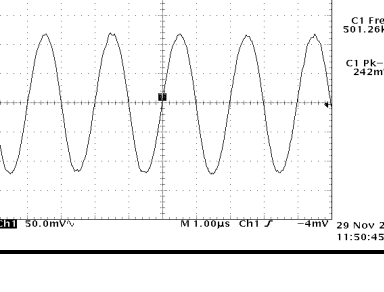
Output Signal Ports	Audio Signal Frequencies	
	1 kHz	2 kHz
AM O/P1	 <p>                     Tek <b>STOP</b> 50.0kS/s 641 Acqs                      C1 Freq <math>\approx 500 \text{ kHz}</math>                      Wfm does not cross ref                      C1 Pk-Pk 2.74 V                      500mV/div M 500<math>\mu</math>s Ch1 1.29 V                      25 Nov 2003 17:45:35                 </p>	 <p>                     Tek <b>STOP</b> 125kS/s 2225 Acqs                      C1 Freq <math>\approx 500 \text{ kHz}</math>                      Wfm does not cross ref                      C1 Pk-Pk 1.12 V                      500mV/div M 200<math>\mu</math>s Ch1 490mV                      29 Nov 2003 11:48:01                 </p>
AM O/P2	 <p>                     Tek <b>STOP</b> 50.0kS/s 142 Acqs                      C1 Freq <math>\approx 500 \text{ kHz}</math>                      Wfm does not cross ref                      C1 Pk-Pk 2.86 V                      500mV/div M 500<math>\mu</math>s Ch1 1.29 V                      25 Nov 2003 17:46:41                 </p>	 <p>                     Tek <b>STOP</b> 125kS/s 2225 Acqs                      C1 Freq <math>\approx 500 \text{ kHz}</math>                      Wfm does not cross ref                      C1 Pk-Pk 1.12 V                      500mV/div M 200<math>\mu</math>s Ch1 490mV                      29 Nov 2003 11:48:01                 </p>
TP1	 <p>                     Tek <b>STOP</b> 500kS/s 224 Acqs                      C1 Freq 96.6464kHz                      Low resolution                      C1 Pk-Pk 14.8mV                      5.00mV/div M 100<math>\mu</math>s Ch1 2.6mV                      25 Nov 2003 17:48:18                 </p>	 <p>                     Tek <b>STOP</b> 250kS/s 9 Acqs                      C1 Freq 19.3205kHz                      Low resolution                      C1 Pk-Pk 19.0mV                      5.00mV/div M 200<math>\mu</math>s Ch1 60.0mV                      29 Nov 2003 11:49:53                 </p>
TP2	 <p>                     Tek <b>STOP</b> 50.0MS/s 60 Acqs                      C1 Freq 499.38kHz                      C1 Pk-Pk 238mV                      50.0mV/div M 1.00<math>\mu</math>s Ch1 0 V                      25 Nov 2003 17:48:51                 </p>	 <p>                     Tek <b>STOP</b> 50.0MS/s 65 Acqs                      C1 Freq 501.26kHz                      C1 Pk-Pk 242mV                      50.0mV/div M 1.00<math>\mu</math>s Ch1 -4mV                      29 Nov 2003 11:50:45                 </p>



Table 3-6 Observe on the variation of amplitude modulation by changing the frequency of audio signal (Continue) ( $V_m = 600 \text{ mV}_{pp}$ ,  $f_c = 500 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).

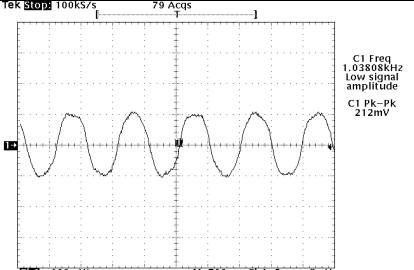
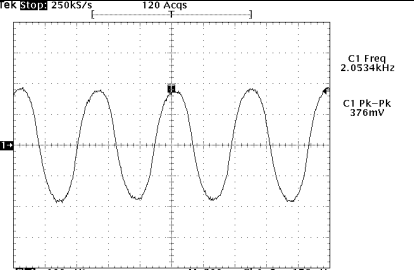
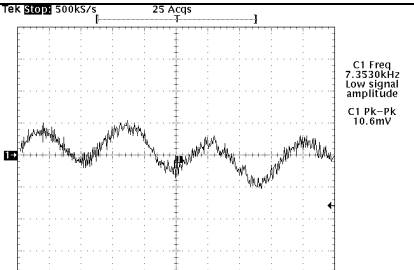
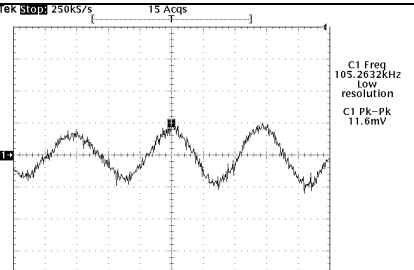
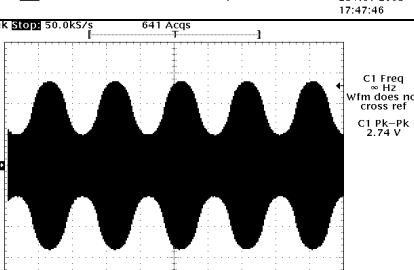
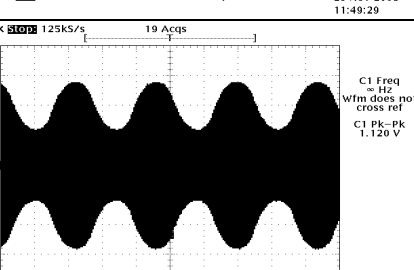
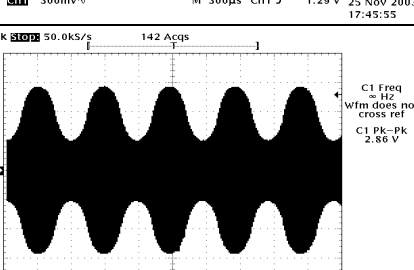
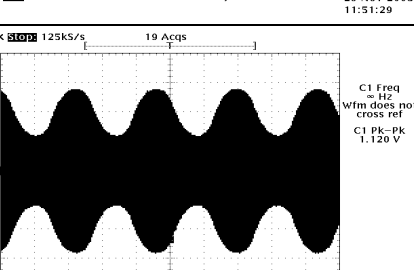
Output Signal Ports	Audio Signal Frequencies	
	1 kHz	2 kHz
TP3		
TP4		
TP5		
TP6		

Table 3-6 Observe on the variation of amplitude modulation by changing the frequency of audio signal (Continue) ( $V_m = 600 \text{ mV}_{pp}$ ,  $f_c = 500 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).

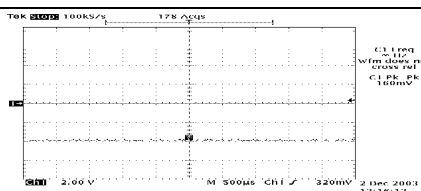
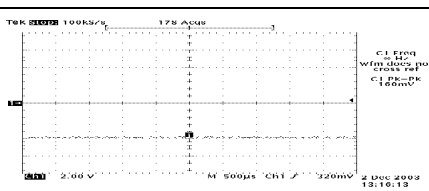
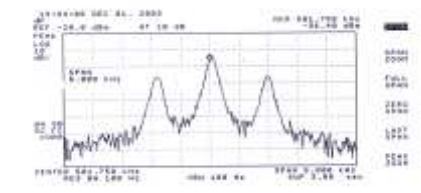
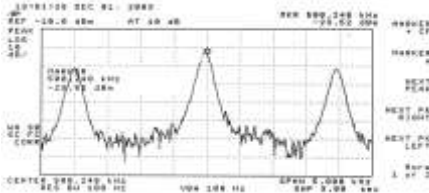
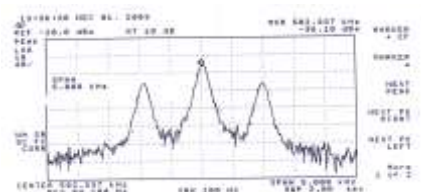
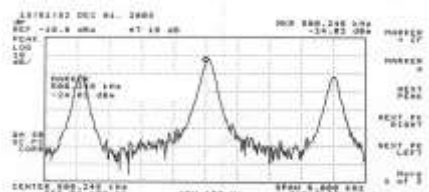
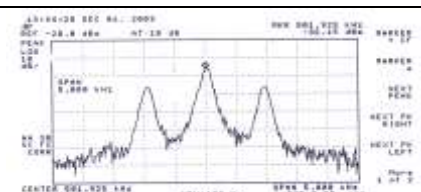
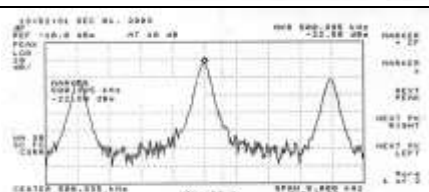
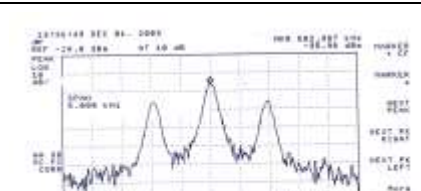
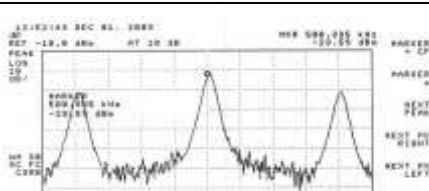
Output Signal Ports	Audio Signal Amplitudes	
	1 kHz	2 kHz
TP7		
AM O/P1 Output Signal Spectrums		
AM O/P2 Output Signal Spectrums		
TP5 Output Signal Spectrums		
TP6 Output Signal Spectrums		
Modulation Index	$E_{\max} = 1.37 \text{ V}$ $E_{\min} = 500 \text{ mV}$ $m = 46.5 \%$	$E_{\max} = 560 \text{ mV}$ $E_{\min} = 200 \text{ mV}$ $m = 47.4 \%$



Table 3-9 Observe on the variation of amplitude modulation by changing the variable resistor  $VR_1$  ( $V_m = 600 \text{ mV}_{pp}$ ,  $f_m = 1 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $f_c = 500 \text{ kHz}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).

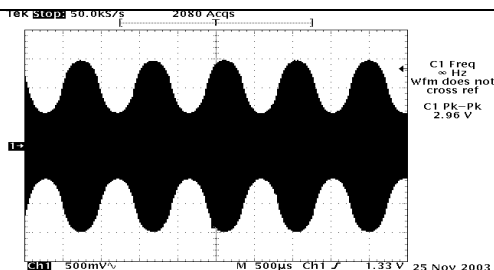
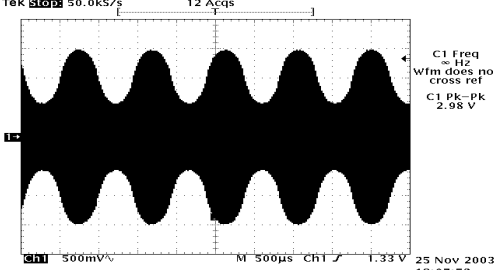
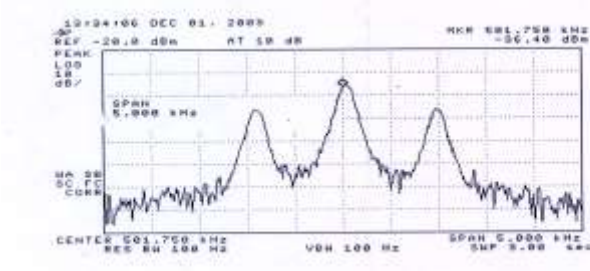
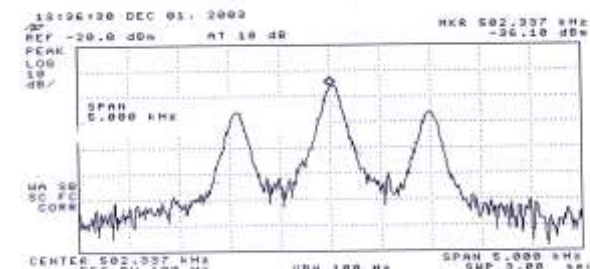
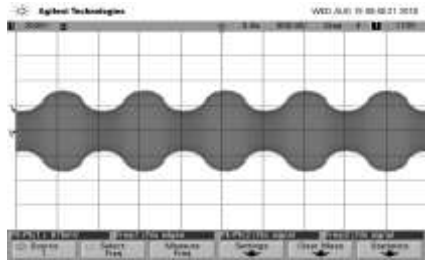
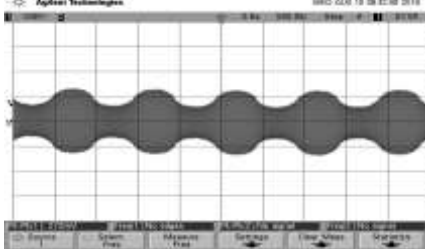
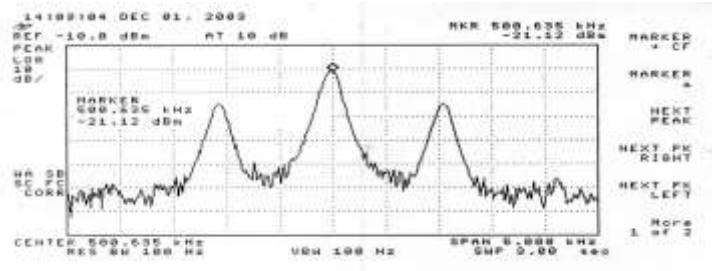
Modulation Index		Output Signal Waveforms	Modulation Percentages
50 %	AM O/P1	 <p>C1 Freq = 500 kHz Wfm does not cross ref C1 Pk-Pk 2.96 V</p>	$E_{\max} = 1.48 \text{ V}$ $E_{\min} = 550 \text{ mV}$ $m = 49.4 \%$
	AM O/P2	 <p>C1 Freq = 500 kHz Wfm does not cross ref C1 Pk-Pk 2.98 V</p>	$E_{\max} = 1.48 \text{ V}$ $E_{\min} = 550 \text{ mV}$ $m = 49.4 \%$
		Output Signal Spectrums	
50 %	AM O/P1		
	AM O/P2		

Table 3-10 Observe on the variation of amplitude modulation by changing the variable resistor VR<sub>2</sub> ( $V_m = 600 \text{ mV}_{pp}$ ,  $f_m = 1 \text{ kHz}$ ,  $V_c = 300 \text{ mV}_{pp}$ ,  $f_c = 500 \text{ kHz}$ ,  $R_{12} = 3.3 \text{ k}\Omega$ ).

Magnitudes of Variable Resistor VR <sub>2</sub>		Output Signal Waveforms	Modulation Percentages
300 $\Omega$	AM O/P1		$E_{\max} = 337.5 \text{ mV}$ $E_{\min} = 173 \text{ mV}$ $m = 32.2 \%$
	AM O/P2		$E_{\max} = 136 \text{ mV}$ $E_{\min} = 67.5 \text{ mV}$ $m = 33.7 \%$
300 $\Omega$	Output Signal Spectrums		
	AM O/P1		
	AM O/P2	